



Donald A. Smith, W3UZM  
 Associate Editor  
 P.O. Box 45  
 Hagerstown, Maryland

# Testing the Heath Mohican (GC-1A) Transistor Communications Receiver

PERHAPS you can imagine the doubts which would build up in your mind if you were to take on the job of writing something good about a one hundred dollar "Communications" receiver. Add to this, that it is transistorized and you've had sour experiences with previously available amateur transistor gear.

After the receiver had been assembled (Heath sells *kits*, you know), which took me about 30 hours, the receiver was ready for alignment. I followed the rather complete and thorough instructions provided. Alignment requires a signal generator (like the Heath SG-7) and a VTVM (like the Heath V-7a). Once aligned, I antenna'd it with the whip which comes with the kit and started tuning to determine the magnitude of the disaster.

HMMM, Well, what do you know? HMMM. HMMMMMMMMMM! Well I'll be darned! By George! Hey! This thing is really something. The advertised specs of 2 microvolts sensitivity (except on the broadcast band), were found to be quite conservative, even on the ten meter band where most receivers are strangely quiet. This little box of parts held its own right alongside of receivers costing up to twice as much. Let's see what makes it tick.

The biggest secret is probably in the front end. After all, if it doesn't have it up front, it doesn't have it. Three transistors are used in the front end. One for rf amplifier, one each for oscillator and mixer. These transistors are not run of the mill jobs, but are good at frequencies up to 100 mc! Thus it's not much

of a problem getting performance up to 30 mc. The way the front end layout was designed helps to keep leads short. The transistors are mounted on shields and the band change switch is installed through these shields.


By using adjustable coils in the front end, plus trimmer capacitors, fairly constant sensitivity across the dial is obtained. This eliminates the "dead spots" that we all have experienced.

What about selectivity? The figures are 3 kc to the half power point (6 db down), which is made possible by the use of "transfilters". These little jobs are unusual in that they do the job of an if transformer, crystal filter and coupling capacitor, but are none of these. They are somewhat similar to a crystal lattice filter in their operation, though not as efficient. They give much better selectivity than could be achieved from standard if transformers, are rugged and never need adjustment! (Though they have been used by the Signal Corps, this is the first commercial application of them).


What's the line up? 10 transistors, 3 germanium diodes, 2 compensating diodes and 1 voltage regulating Zener diode are used. This gives an rf stage, a separate oscillator and mixer, three if stages, a diode detector, an audio driver and a push-pull output stage. A separate transistor is used for the variable BFO. Diodes are used for automatic noise limiter and AVC.

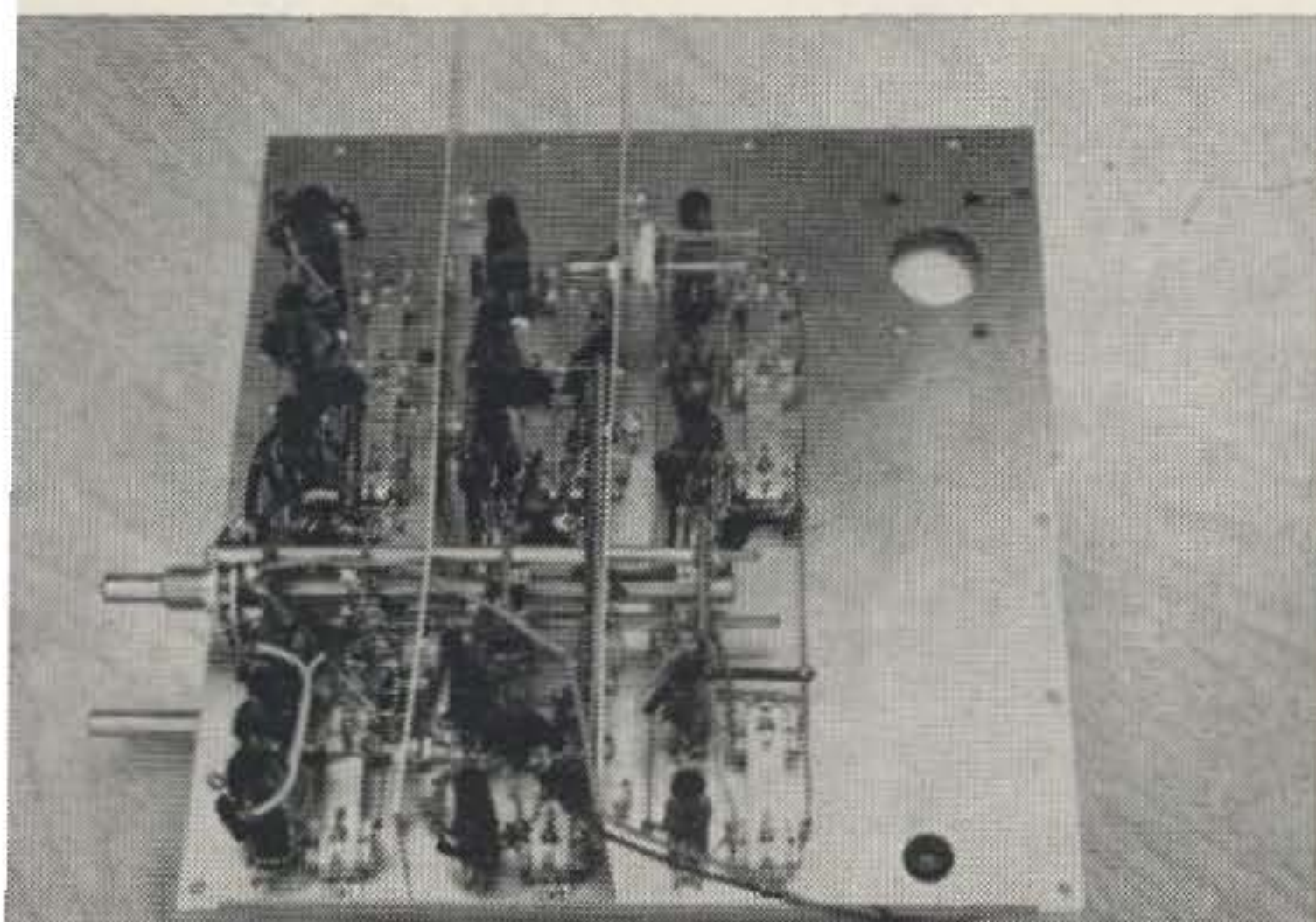And that's not all! A Zener diode is used






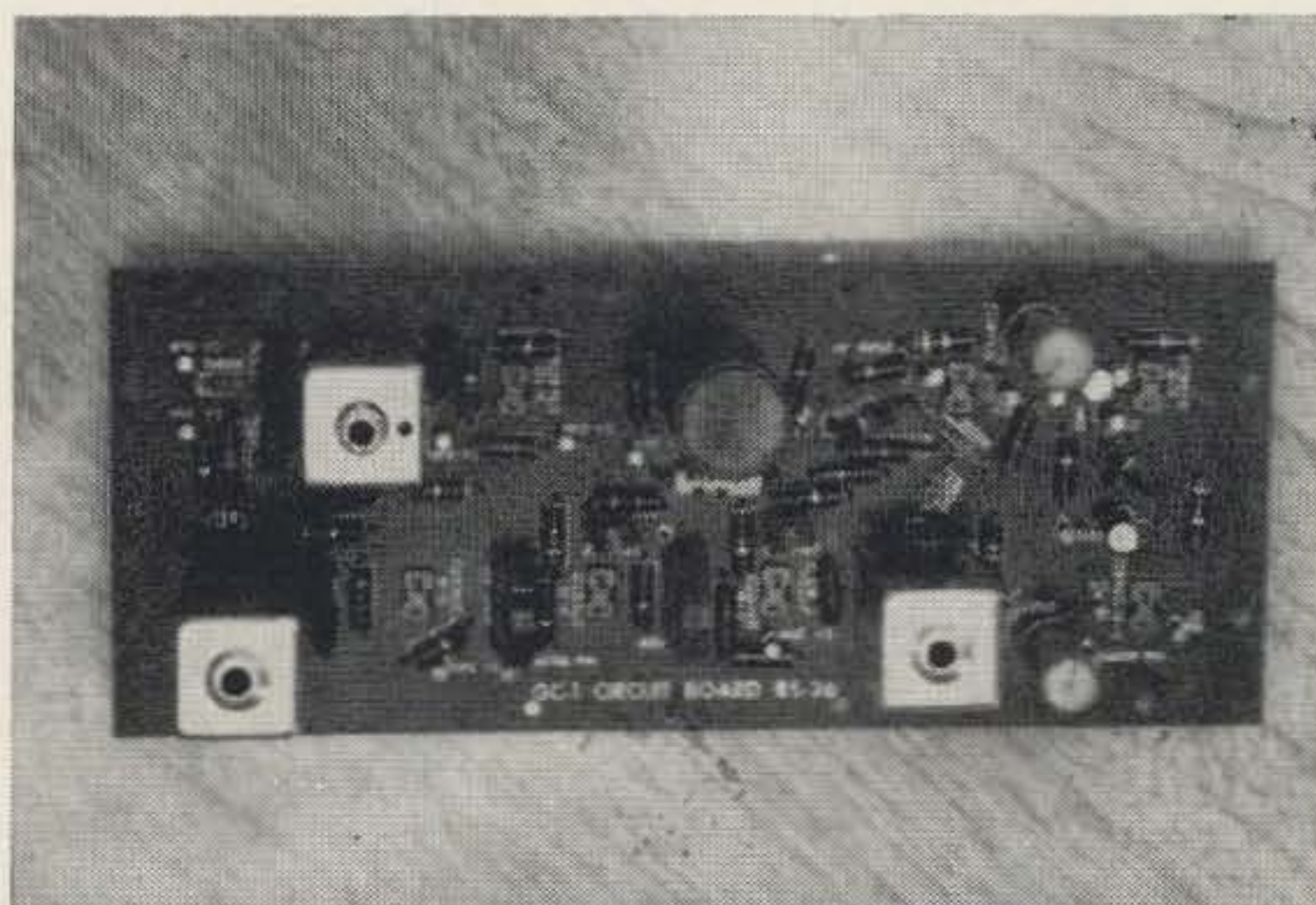
The *rf* section is constructed first. Note that all parts are mounted on a flat sheet, simplifying construction.



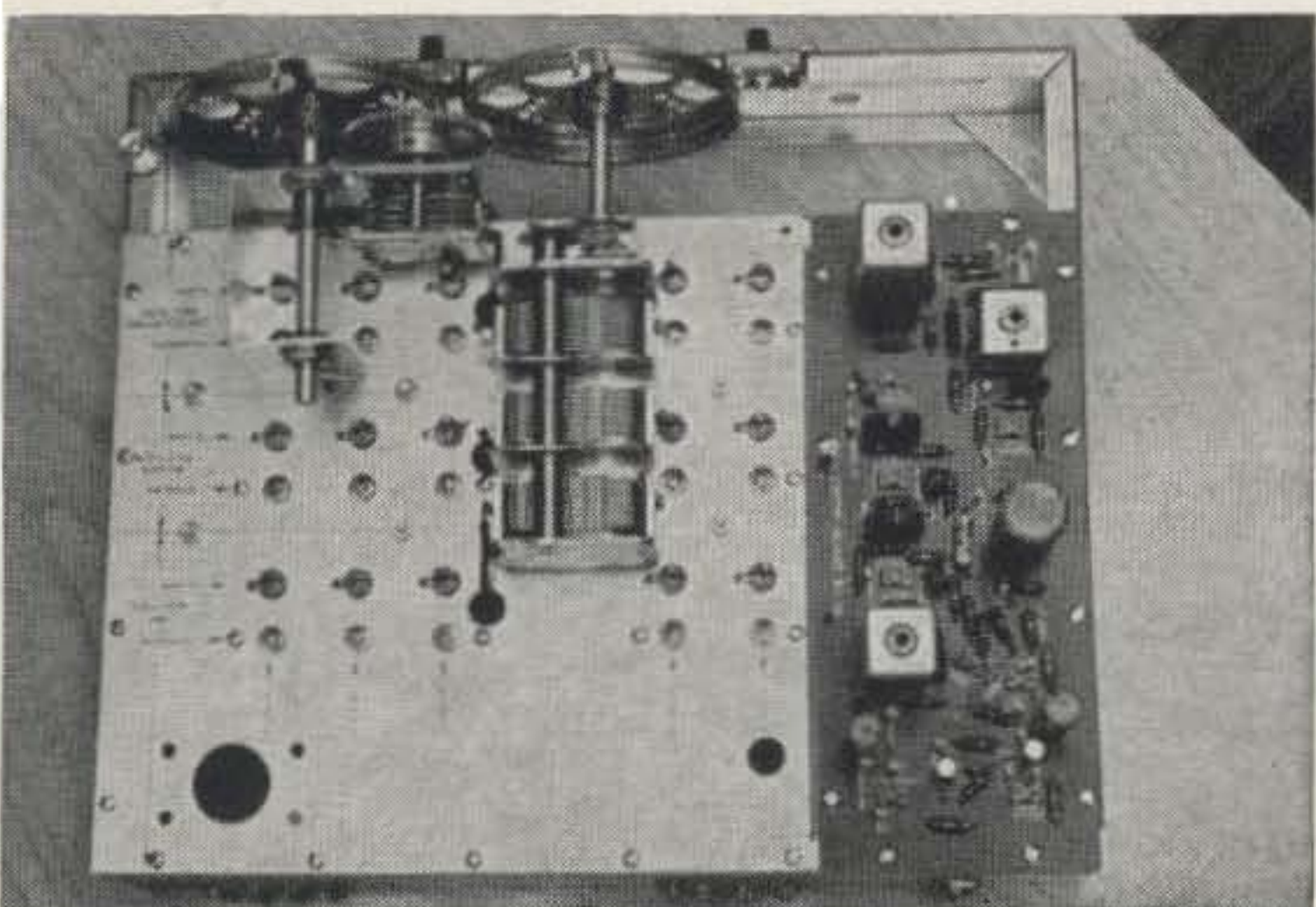
A printed circuit board is used for mounting and wiring of the *if* and audio sections of the receiver.



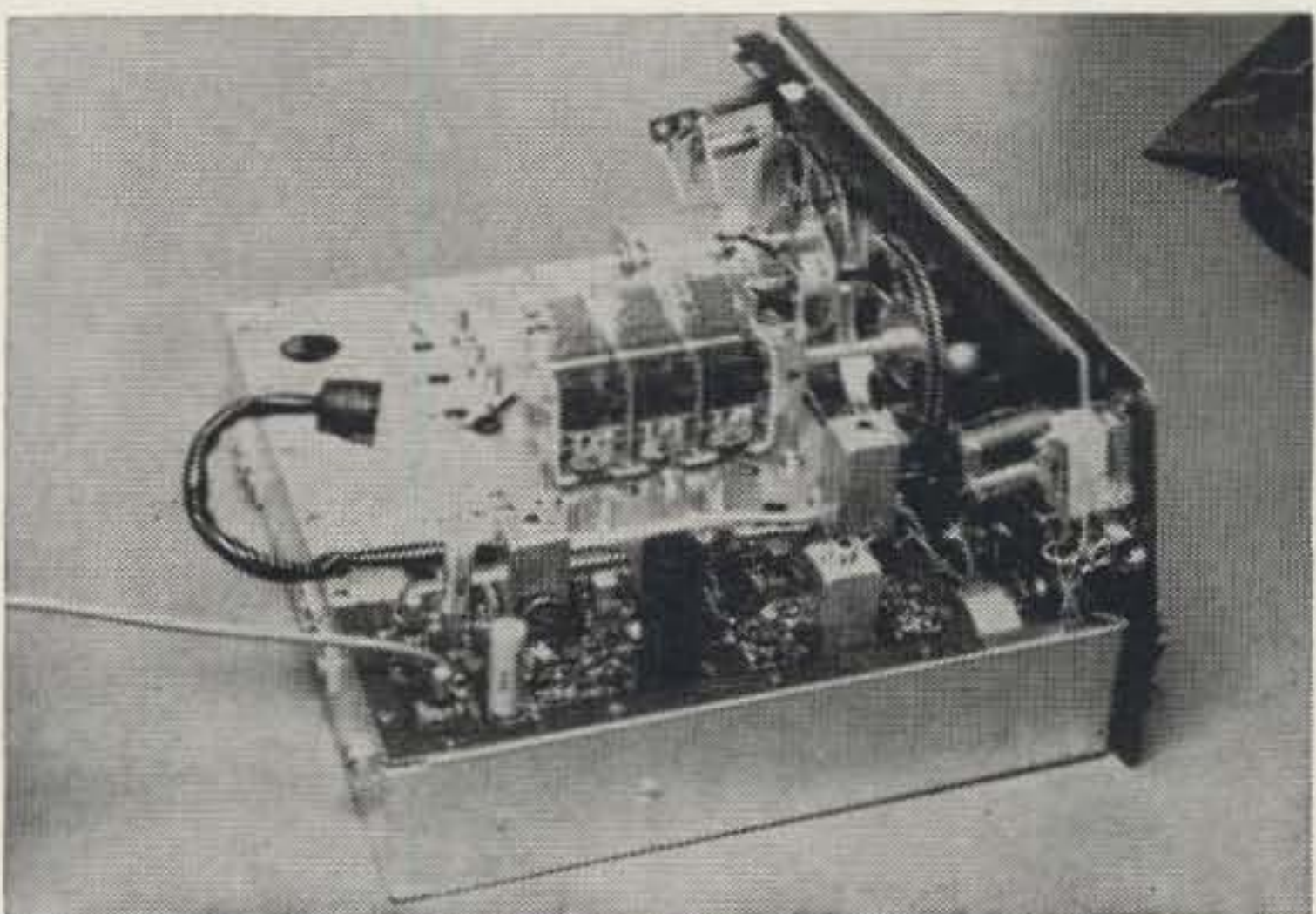
The completed *rf* section and the printed circuit board are mounted on the main chassis and wired to each other.



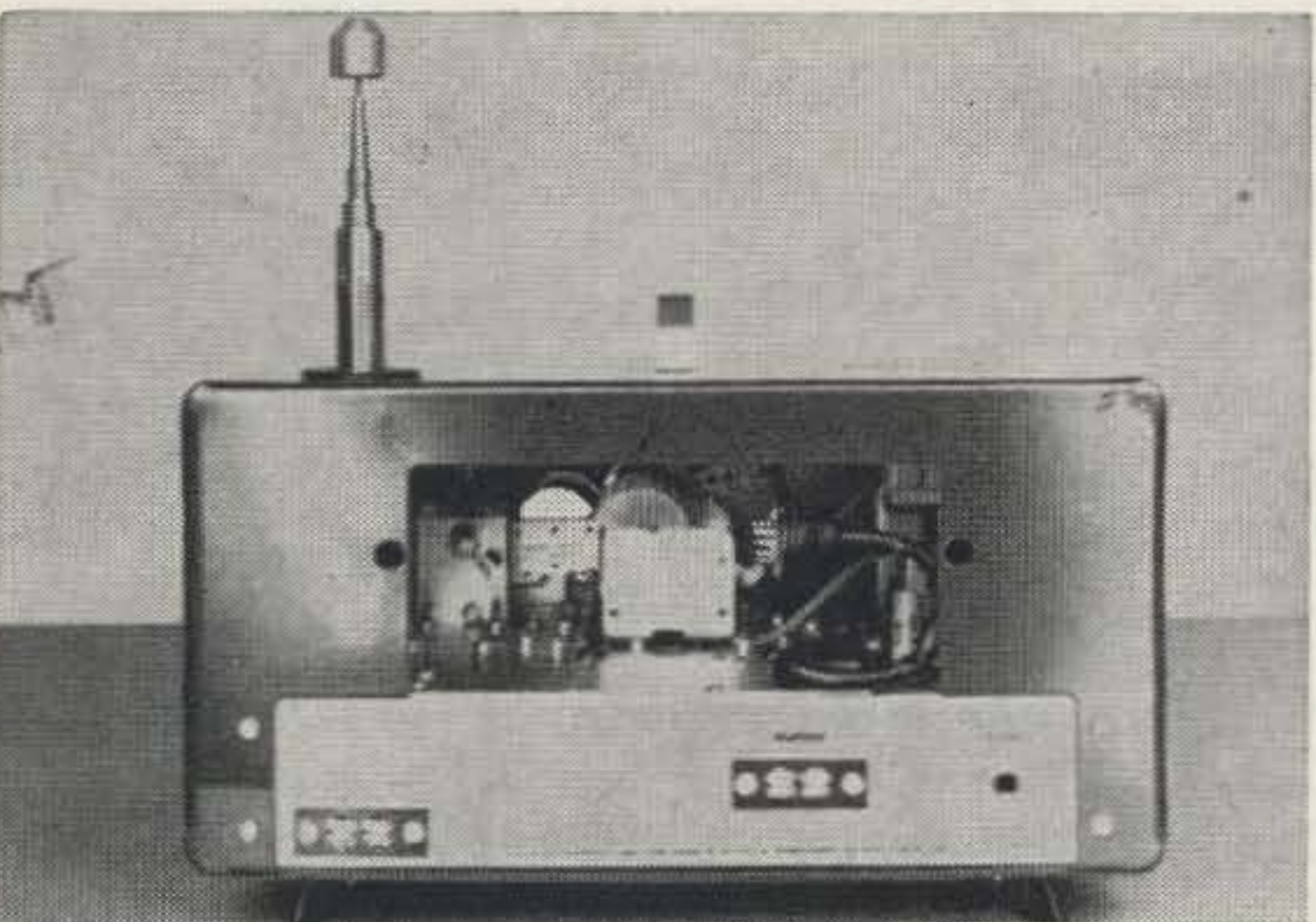Completed receiver, cabinet removed. Wire going off to the left connects to speaker mounted in cabinet. Large hole in upper left corner is where "Whip" antenna goes.



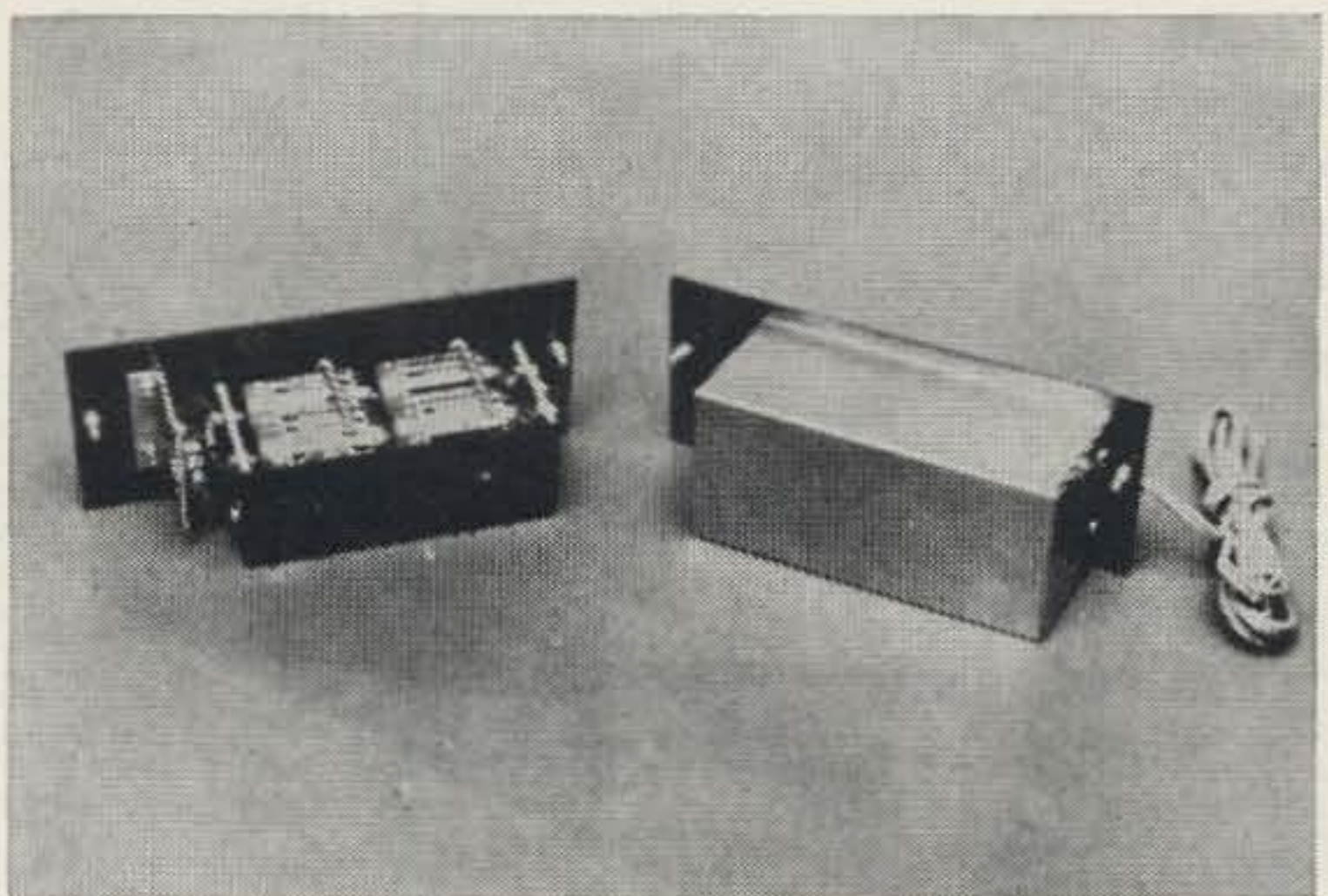Rear of completed receiver with power supply removed. Plug shown in the cut-out, is power plug which is plugged into power supply.



Battery supply on left is furnished with the kit, (less batteries). The supply on the right is *ac* operated supply which is purchased separately, if desired.

as a voltage regulator for the local oscillator. -6.8 volts is applied from the diode to the transistor oscillator base, holding drift down to a *very* low amount. It is the nature of a Zener diode that when a voltage is applied to the diode backwards, reverse current is very low. If the voltage should exceed this amount, the breakdown potential of the diode occurs

and the reverse current through the diode increases, bring the voltage back down to the pre-set amount, which is -6.8v in our case.

Another interesting circuit is in the push-pull audio output stage. Two 1N2326 compensating diodes are used, one in each of the output stages, connected to the transistor base circuits. These diodes have a negative tem-



